

CSE 200: Online-1 on L^AT_EX (B1)

Time: 50 Minutes
Total Marks: 50

Instructions

- Reproduce the following article using L^AT_EX exactly as it is.
- You do not need to reproduce this instruction page.
- Ensure that all text formatting, lists, nested lists, tables, equations, figures, code listings, footnotes, hyperlinks, citations, and references are implemented as presented in the article using appropriate L^AT_EX commands.
- You may use offline materials and online searching, but the use of AI tools is prohibited.
- Exact line breaks, page breaks, and float positions are not required. However, the submitted document should closely resemble the supplied article and must compile successfully.

Mark Distribution

Topic	Marks
Document Structure, Title, Authors & Affiliations	4
Lists, Nested Lists, Text Formatting & Colors	4
Laplace-transform Equations & Derivations	8
RC-circuit Equations, Alignments & Transfer Function	10
Multirow and Multicolumn Table	8
Wrapped and Rotated Figure, Caption & Label	4
Python Code Listing and Syntax Formatting	5
Cross-references	2
Footnote	1
Hyperlink	1
Citations & Bibliography	1
Overall Presentation & Successful Compilation	2
Total	50

Laplace Analysis and Applications

Pierre-Simon Laplace¹, Oliver Heaviside², and Gustav Robert Kirchhoff³

¹Académie des Sciences, Paris, France

²Royal Society, London, United Kingdom

³University of Heidelberg, Heidelberg, Germany

1 From Functions to Transforms

1.1 The Laplace Transform

Let $f(t)$ be a function defined for $t \geq 0$. Its Laplace transform is defined by

$$\mathcal{L}\{f(t)\} = F(s) = \int_0^\infty e^{-st} f(t) dt, \quad s > 0. \quad (1)$$

The transform changes a function of time into a function of the new variable s .¹ Symbolically,

$$f(t) \xrightarrow{\mathcal{L}} F(s).$$

The inverse Laplace transform reverses this process:

$$f(t) = \mathcal{L}^{-1}\{F(s)\}. \quad (2)$$

The main purpose of the method is to replace differentiation and integration in the time domain by simpler algebraic operations in the transform domain [1]. A concise overview is available from the [Laplace Transform entry on MathWorld](#).

1.2 A Simple Example

For the constant function $f(t) = 1$,

$$\begin{aligned} \mathcal{L}\{1\} &= \int_0^\infty e^{-st} dt \\ &= \left[-\frac{1}{s} e^{-st} \right]_0^\infty \\ &= \frac{1}{s}. \end{aligned} \quad (3)$$

Similarly,

$$\mathcal{L}\{t\} = \frac{1}{s^2}, \quad \mathcal{L}\{t^2\} = \frac{2}{s^3}. \quad (4)$$

¹The variable s is commonly interpreted as a complex-frequency variable.

2 Common Transform Equations

Table 1 lists several frequently used Laplace-transform equations.

Table 1: Selected Laplace-transform equations.

Family	Transform Equation		Condition
	Time function	Laplace transform	
Algebraic	1	$\frac{1}{s}$	$s > 0$
	t	$\frac{1}{s^2}$	$s > 0$
	t^n	$\frac{n!}{s^{n+1}}$	$n = 0, 1, 2, \dots$
Exponential	e^{at}	$\frac{1}{s-a}$	$s > a$
	e^{-at}	$\frac{1}{s+a}$	$s > -a$
Oscillatory	$\sin(\omega t)$	$\frac{\omega}{s^2 + \omega^2}$	$\omega > 0$
	$\cos(\omega t)$	$\frac{s}{s^2 + \omega^2}$	$\omega > 0$
Unit-step function $u(t-a)$		$\frac{e^{-as}}{s}$	$a > 0$

The formulas in Table 1 allow many functions to be transformed without repeatedly evaluating improper integrals.

3 Application to an RC Circuit

Circuit Model

Figure 1 shows a simple resistor--capacitor circuit connected to an input voltage source. The resistor limits the current, while the capacitor stores electrical energy.

For a resistor R and capacitor C , Kirchhoff's voltage law gives

$$RC \frac{dv_C(t)}{dt} + v_C(t) = v_{in}(t), \quad (5)$$

where $v_C(t)$ is the voltage across the capacitor.

Assuming $v_C(0) = 0$, taking the Laplace transform of Equation (5) gives

$$\begin{aligned}
 RC [sV_C(s) - v_C(0)] + V_C(s) &= V_{in}(s), \\
 \Rightarrow RCsV_C(s) + V_C(s) &= V_{in}(s), \\
 \Rightarrow V_C(s)(RCs + 1) &= V_{in}(s).
 \end{aligned} \quad (6)$$

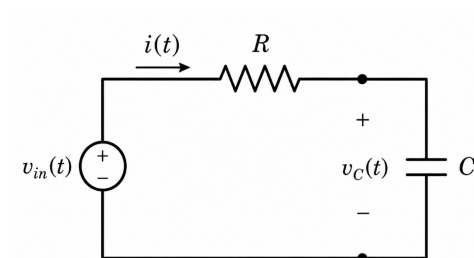


Figure 1: A simple series RC circuit.

The transfer function is therefore

$$H(s) = \frac{V_C(s)}{V_{\text{in}}(s)} = \frac{1}{RCs + 1}. \quad (7)$$

For a constant input V_0 ,

$$V_{\text{in}}(s) = \frac{V_0}{s}.$$

Thus,

$$V_C(s) = \frac{V_0}{s(RCs + 1)}. \quad (8)$$

Taking the inverse transform gives

$$v_C(t) = V_0 \left(1 - e^{-t/(RC)} \right). \quad (9)$$

The quantity $\tau = RC$ is called the time constant of the circuit. A larger value of τ causes the capacitor to charge more slowly [2].

4 How Laplace Analysis Is Used

The Laplace transform is useful in many areas:

Differential equations $\oplus$ initial conditions are included automatically;

$\oplus$ derivatives become algebraic expressions.

Electrical circuits $\oplus$ voltages and currents are studied in the s -domain;

$\oplus$ components lead to transfer functions.

Control and signal systems $\oplus$ stability can be studied through poles;

$\oplus$ common test inputs include:

▷ the unit-step input;

▷ the impulse input;

▷ sinusoidal inputs.

In the time domain, a system may be described by a differential equation, whereas in the Laplace domain, the same system is often described by a rational algebraic expression.

5 A Short Python Implementation

Listing 1 evaluates the capacitor voltage at a finite set of time instants using an external Python file.

```

1 from math import exp
2
3
4 def rc_response(resistance, capacitance, input_voltage, times):
5     """Return capacitor-voltage samples for an RC step input."""
6     if resistance <= 0 or capacitance <= 0:
7         raise ValueError("R and C must be positive")
8
9     tau = resistance * capacitance
10    values = []
11
12    for time in times:
13        voltage = input_voltage * (1 - exp(-time / tau))
14        values.append(voltage)
15
16    return values
17
18
19 times = [0.0, 0.5, 1.0, 2.0]
20 print(rc_response(2.0, 0.5, 5.0, times))

```

Listing 1: Computing samples of the RC step response.

Equation (9) and Listing 1 describe the same computation.

References

- [1] E. Kreyszig, *Advanced Engineering Mathematics*, 10th ed. John Wiley & Sons, 2011.
- [2] K. Ogata, *Modern Control Engineering*, 5th ed. Prentice Hall, 2010.